
Hardware Tutorial:

1- Energy Harvesting Unit

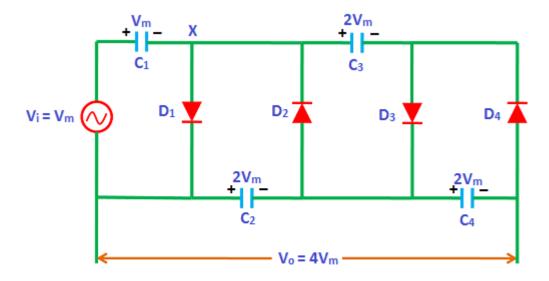Let's start by building the harvesting unit which is composed of two main parts the voltage multiplier and a supercapacitor to store the energy. The output of the voltage multiplier is a DC rectified and multiplied version of the incoming signal. In our design we used a four-stage voltage multiplier with this architecture.



Voltage Quadrupler

Fig1: Single ended voltage multiplier

Link for more information on voltage multipliers:

https://www.physics-and-radio-electronics.com/electronic-devices-and-circuits/rectifier/voltagemultipliers-voltagedoubler-tripler-quadrupler.html

Note1: The DC voltage at the output of the voltage regulator is given by:

Vo = N*(Vmax-Vth)

Where N is the number of stages of the voltage multiplier (4 in our case), Vmax is the amplitude of the incoming signal, and Vth is the threshold voltage of the diodes being used.

Note2: The DC output of the voltage multiplier can be negative or positive depending on the orientation of the diodes.

Note3: The voltage multiplier acts as an envelope detector (low-pass filter); thus, when transmitting a PWM signal the output of the voltage regulator will look like the envelope of a sinusoidal signal that turns on and off. Like in the image below. If lower capacitances in the voltage multiplier are used the discharging time can be decreased; however, this will also cause a small ripple to appear.

Note4: The schematic in Fig.1 shows a single ended voltage multiplier for simplicity. However, since the output of the piezo electric is differential in our circuit design, we have a differential voltage multiplier which also includes a mirror image of the schematic in Fig1. (You will find the full architecture in our PCB layout)


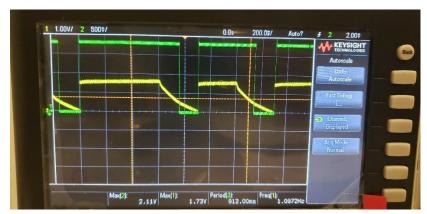


Fig2: Yellow curve is the PWM signal after the voltage regulator. Green curve is the Schmitt triggered version of the yellow signal.

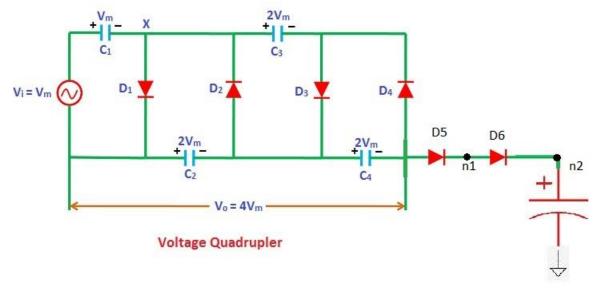Connect the output of the rectifier to the supercapacitor (10000 pF) via two diodes in series like the image below.



2- Downlink Decoder

The decoder in our circuit is composed by a level shifter (TXB0302) fig4, which incorporates a Schmitt Trigger, and a pull-down resistor that is turned on by the MCU(MSP430G2553) when decoding is desired. This part of the circuit converts the output of the PWM signal into a nice clean square wave that can be decoded by the MCU. The reason for the pull-down resistor is to fasten the discharging time of the voltage regulator's capacitors and improve

SNR. The level shifter shifts the signal to a point where that can be detected for the MCU. The output of the level shifter is the green curve in fig2.

Note1: The used MCU incorporates a Schmitt trigger at its input; thus, we could have used only a level shifter.

Note2: The level shifter output is shifted up to the voltage fed into VccB



Fig4: Level shifter TXB0302

Connections:

The level shifter is connected to the rest of the circuit as follows. The junction between diodes D5 and D6 is connected to both VccA and A1. VccB is connected to the output of the voltage regulator. B1 is the output of the level shifter so it is connected the pin 1.1 of our MCU. The OE pin is connected to any pin of our MCU that outputs a constant voltage when it is on and ready to decode. Finally, GND is connected to ground.

Note: The output enable should also be connected to GND via a 47Kohm resistor as suggested by Texas Instruments.

3- Voltage Regulator:

A voltage regulator is needed in our circuit in order to drive the MCU and level shifter with a constant and stable voltage. The voltage regulator used was a lp5900sd(1.8V) because we want to exploit our MCU capability to operate when driven at its minimum voltage of 1.6V.



Fig5: lp5900SD

Connections:

The voltage regulator is connected to the rest of the circuit as follows. Ven and Vin are both connected to the positive end of the supercapacitor. Vout is connected to the VccB pin of the level shifter and to the 3.3V pin of our MCU. Finally, GND is connected to ground.

Note1: Vout and Vin both need a 0.47nF bypass capacitor as described in the image below.


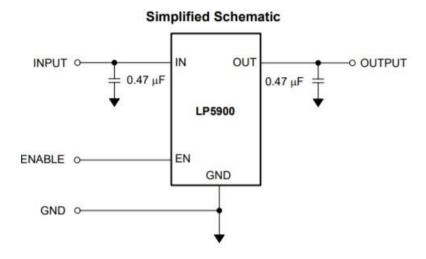


Fig6: LP5900 connections

Note2: If the Ven is higher than 1.2 V the LP5900 will activate and it will saturate at approximately 1.8V when the Vin reaches values higher than 1.8V.

4- Backscatter switches:

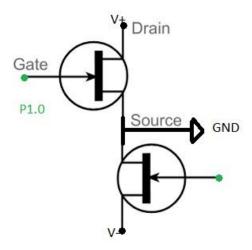Note1: The backscatter switches consist of two N-channel MOSFETs connected in series sharing a common ground. Their sources are connected to each other and to ground. Their gates are connected to the same pin of the MCU (pin 1.0) which turns them on and off. Switching between reflective and absorptive state. The drain of each MOSFET is connected to one terminal of the piezo.




5- Impedance Matching Network:

The piezo electric source has a characteristic impedance. Thus, in order to ensure maximum power transfer to our circuit we added an impedance matching network. We used an L shape network composed by only inductors and capacitors. We used the E4990A Impedance analyzer to measure the impedance of the source and load.

The PCB design is shown below:

PCB layout link:

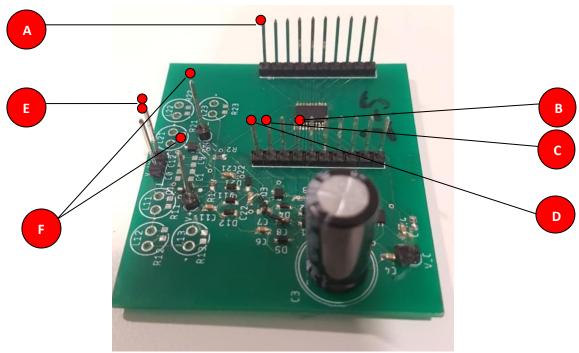

Note that the PCB does not include the impedance matching circuit, but still the PCB can power up the MCU and control the switching of MOSFETs if the super-capacitor can charge up to at least 2.5V from the differential PWM input signal.

The details for inputs and outputs are given below:

- This pin is the common ground for the entire PCB. Use this pin as a reference when measuring voltages across different components using oscilloscope.
- This pin will receive the envelop of the PWM signal in the form of a square wave which is the output of the level-shifter. If this pin shows a different waveform then check the level shifter and see if it is working properly.
- This pin will output the signal which will control the switching of mosfets. The output of this pin depends entirely on the decoding algorithm in the MCU and also on the input from pin "B"
- This pin is the VCC input to the MCU. If the voltage on this pin is lower than 1.8V then the MCU will not power up.
- These set of pins will be used to input the differential PWM signal from the piezoelectric device. Use these pins only after you have populated the PCB will all the components which are required for impedance matching
- These set of pins can also be used to input the differential PWM signal. You can use these pins even if you don't have the impedance matching circuit